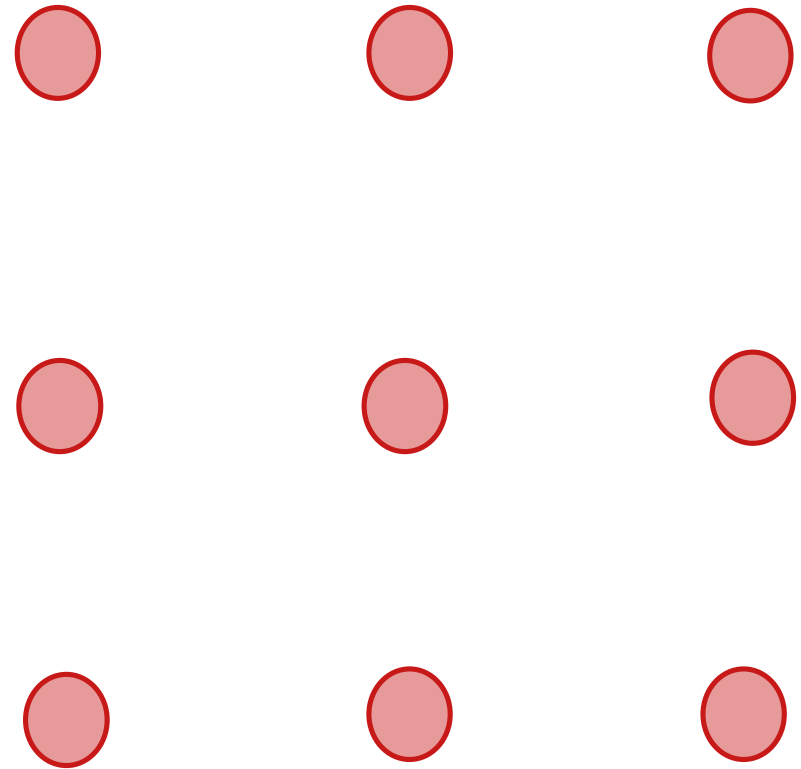


Power Grid Pad Assignment & Design

- John Cohn & Sambasivan Narayan
IBM, Essex Junction


Power Distribution: C4 Pads

- Interface to the external World
- Connect to Pins on the back of a chip




Power Distribution: Loads

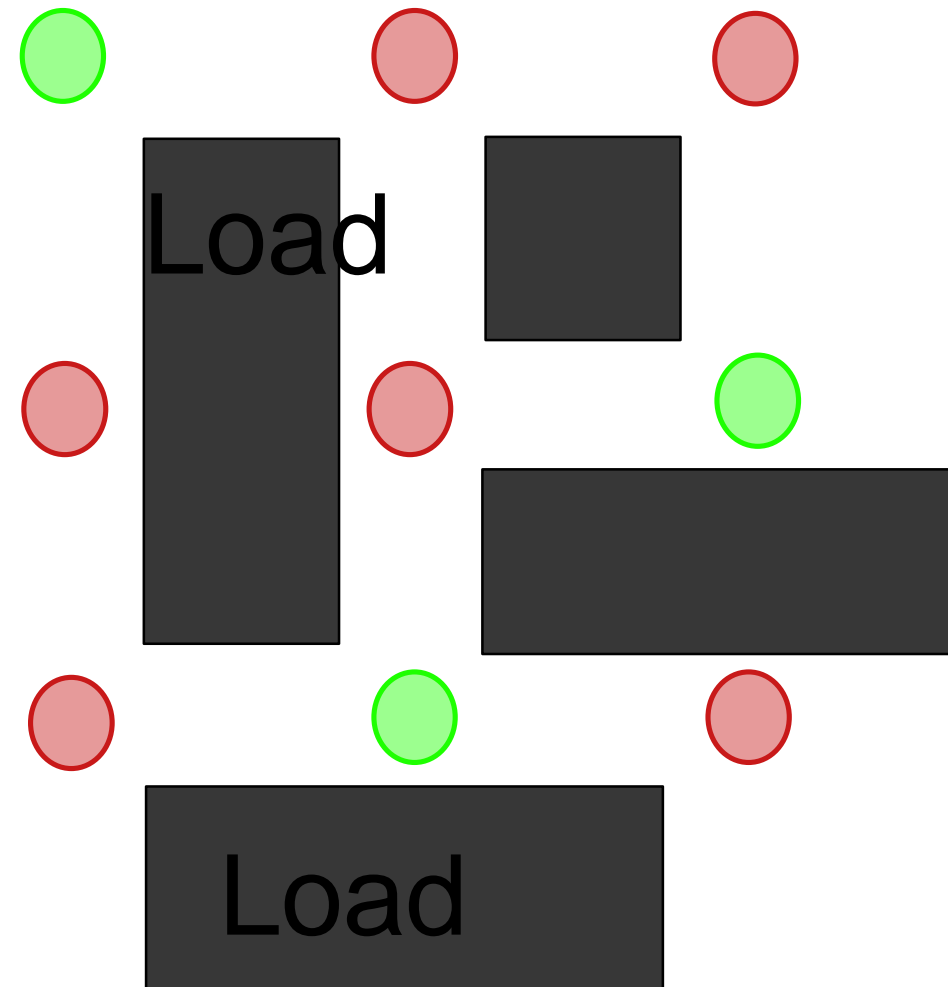- Perform various logical operations
- Pads assigned for Inputs & Outputs (**green**)
- Need power supply for operation




Power Distribution: Power Grid

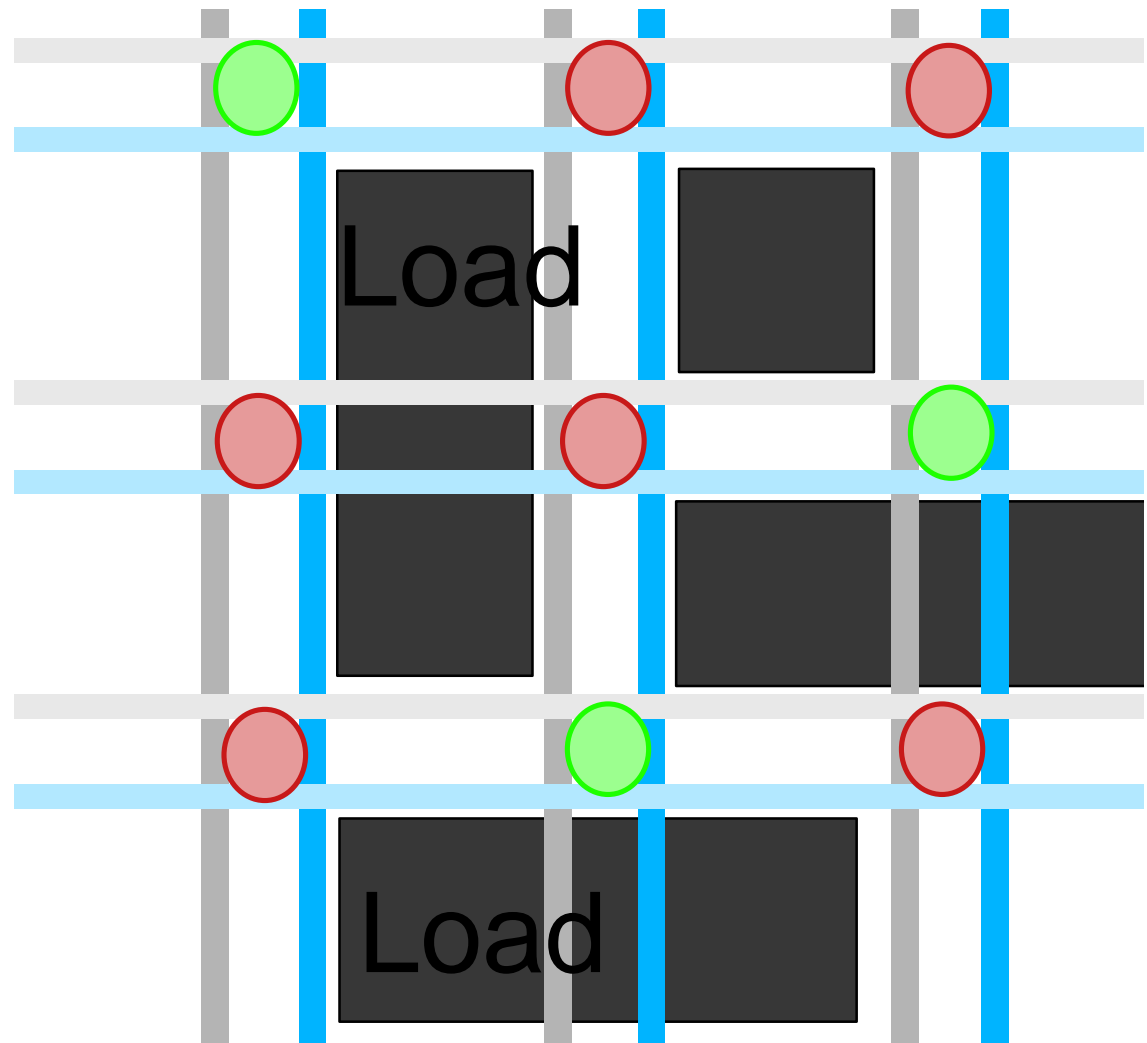- Grey & Blue different power levels (say GND & VDD)
- Different metal levels for Horizontal & Vertical,
- Load connects to lowest metal, pads to the highest
- Load contributes "demand" to both levels



Motivation

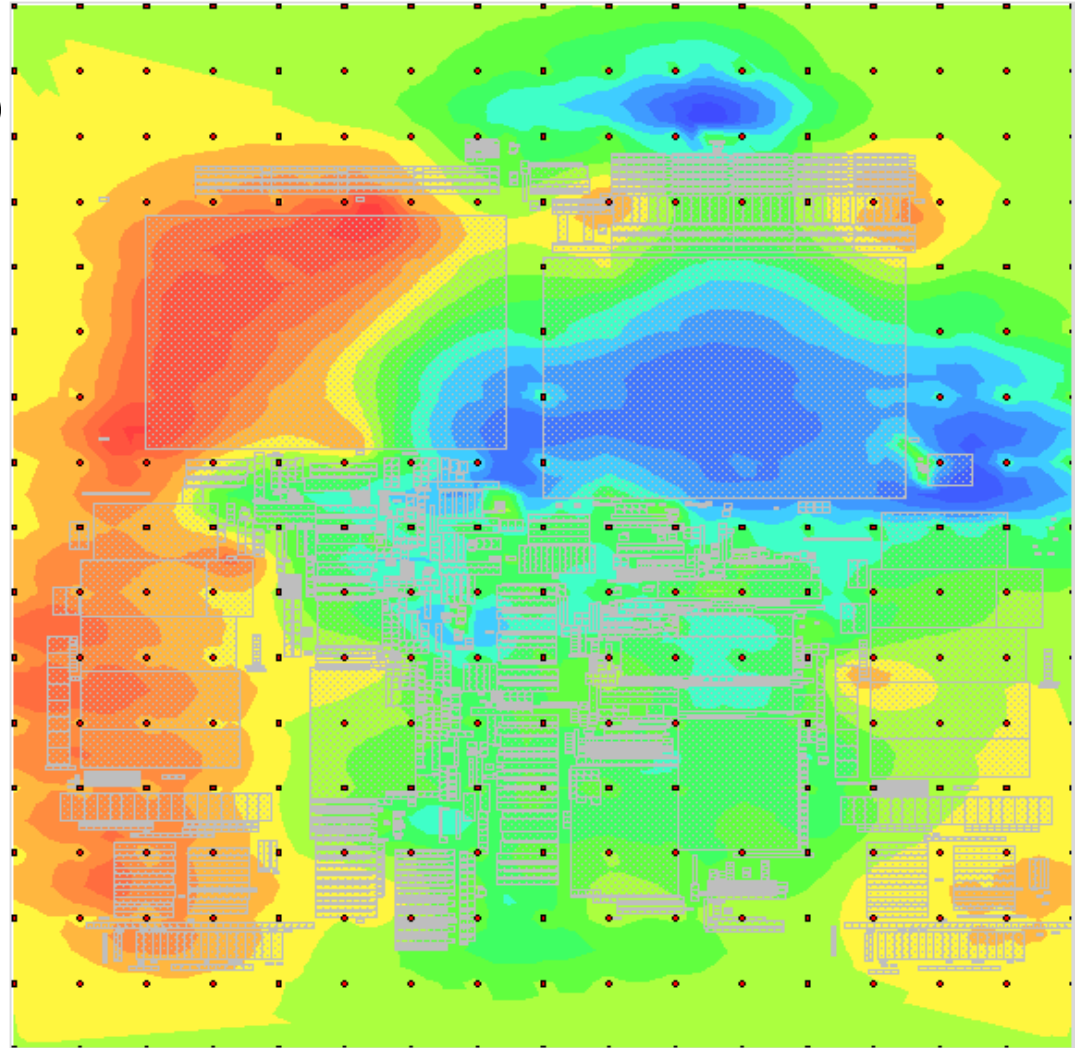- Shows thermal map of VDD power
- Red areas show drop in voltage
- Blue areas have adequate voltage supply




Problem Statement

Assign the available C4 pads, such that each C4 pad has a unique voltage level associated with it, or is unassigned, such that the demands from all the nodes is satisfied

Modelling

- Decoupling the different power levels

Available Pads


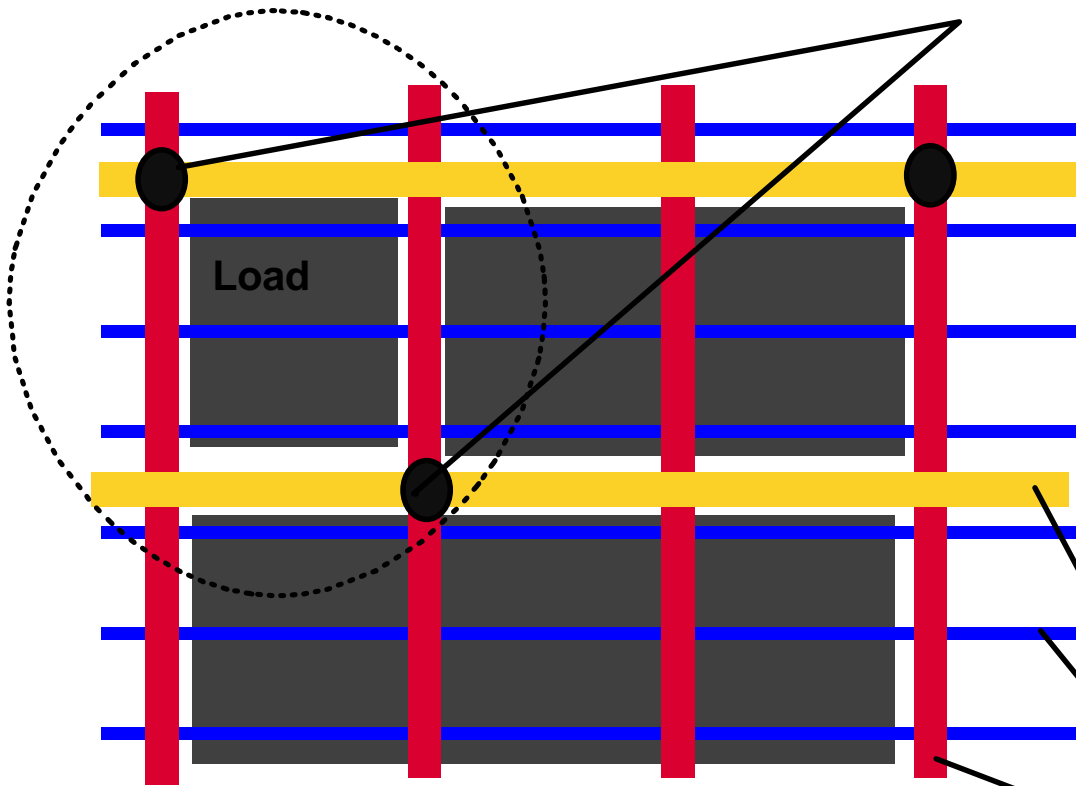


Different Metal levels

Modelling

- Metal Wires: Linear elements (resistors)
 - ▶ Value depends on size of the wire
- Load Demands: Current Sources
- Pads: Constant Voltage Sources
- Intersection between metal wires: vertices in resistor grid

Modelling

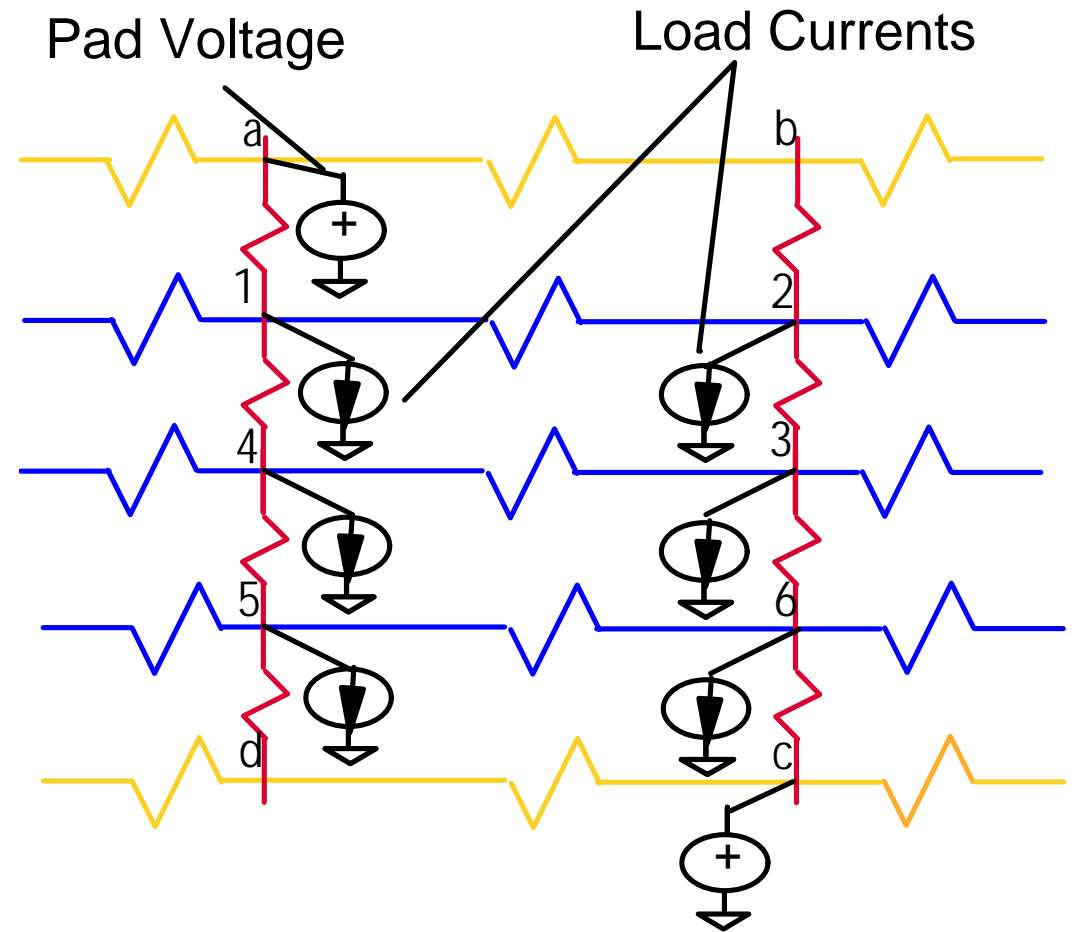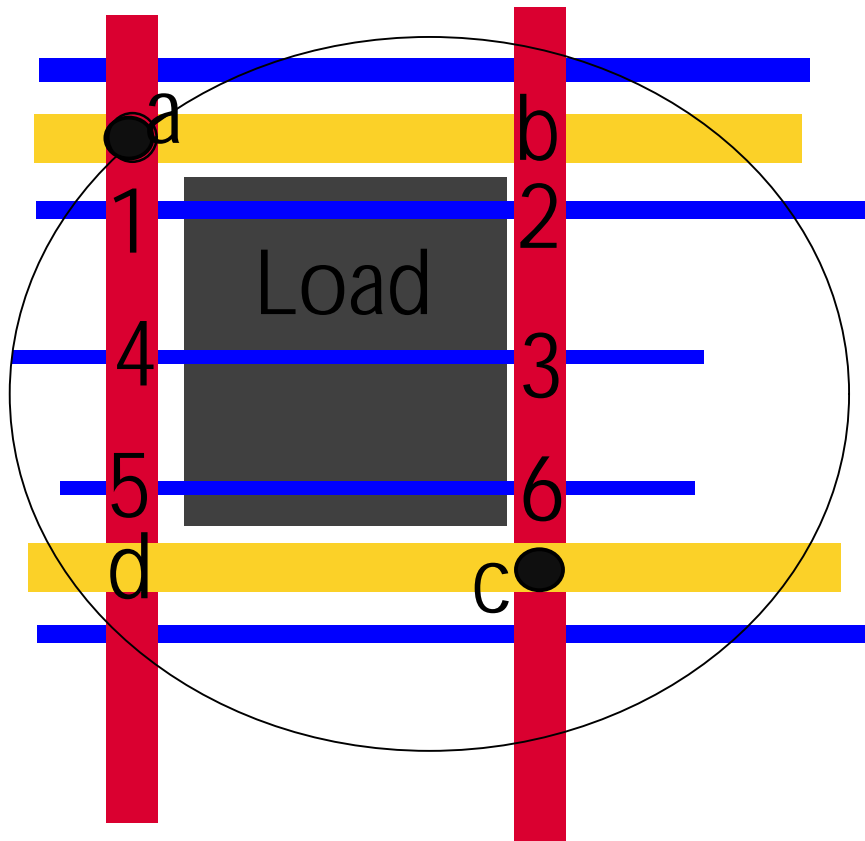


Circuit Analysis: Review

- Kirchoff's Voltage Law: $\sum V_i = 0$
 - ▶ Sum of voltages around a loop is zero
- Ohm's law: $GV = I$
 - ▶ Current through a linear element proportional to voltage across it
- Kirchoff's Current Law: $\sum I_i = 0$
 - ▶ Total current at any node is zero

Circuit Analysis: Example

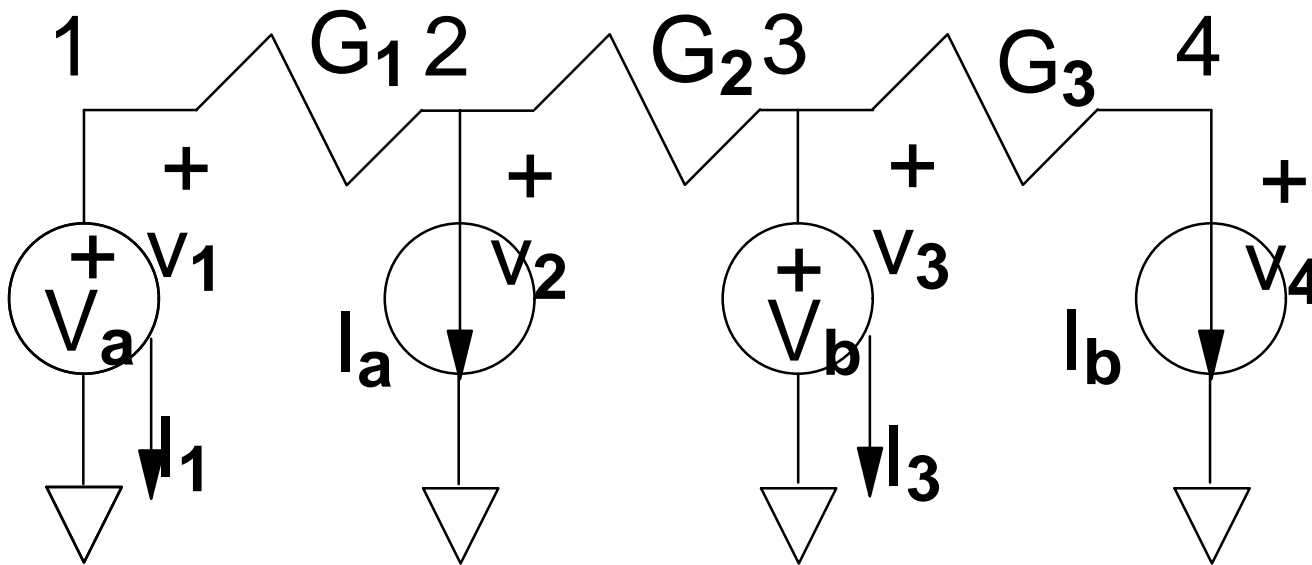- Circuit with 4 unknowns: V_1, V_2, V_3, V_4 ,
- Current sources add unknowns: I_1 & I_3




Circuit Analysis: Example

- KVL gives us

$$V_1 = V_a$$


$$V_3 = V_b$$

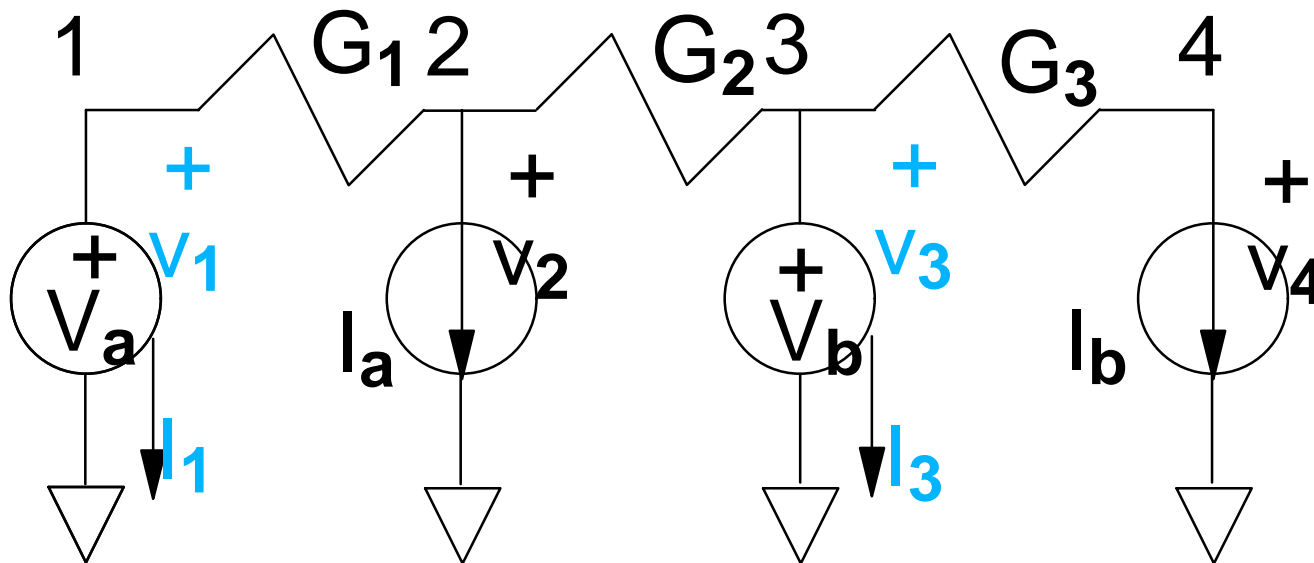

Circuit Analysis: Example

- Applying KCL at node 1:


$$+I_1 + (V_1 - V_2)G_1 = 0$$

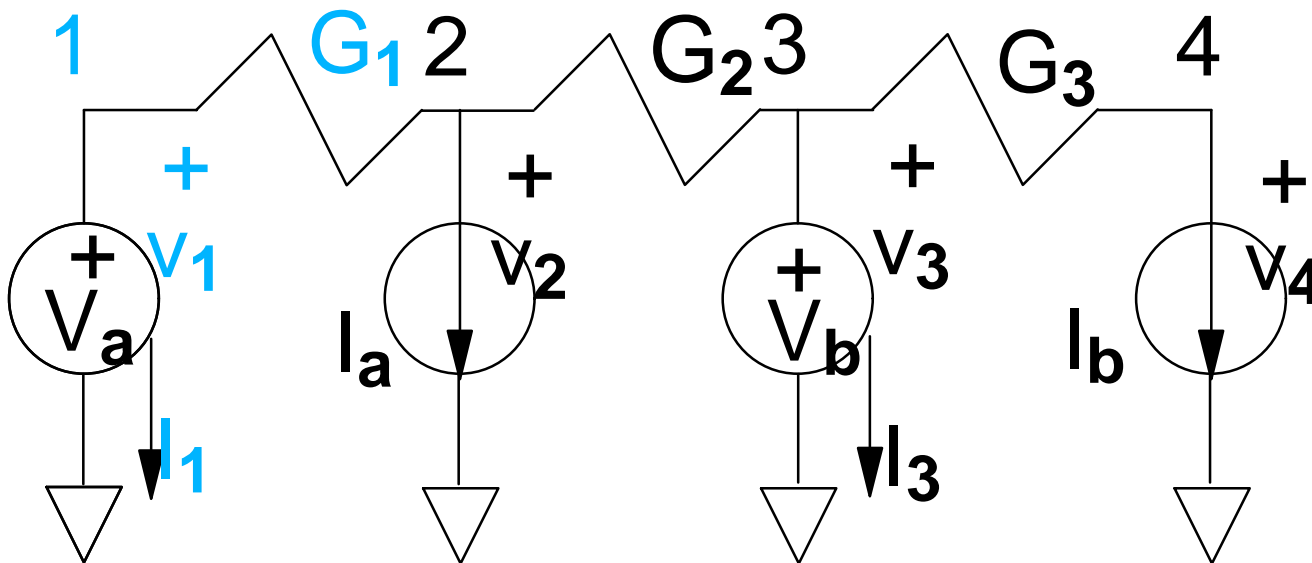

Circuit Analysis: Example

- Applying KCL at node 3

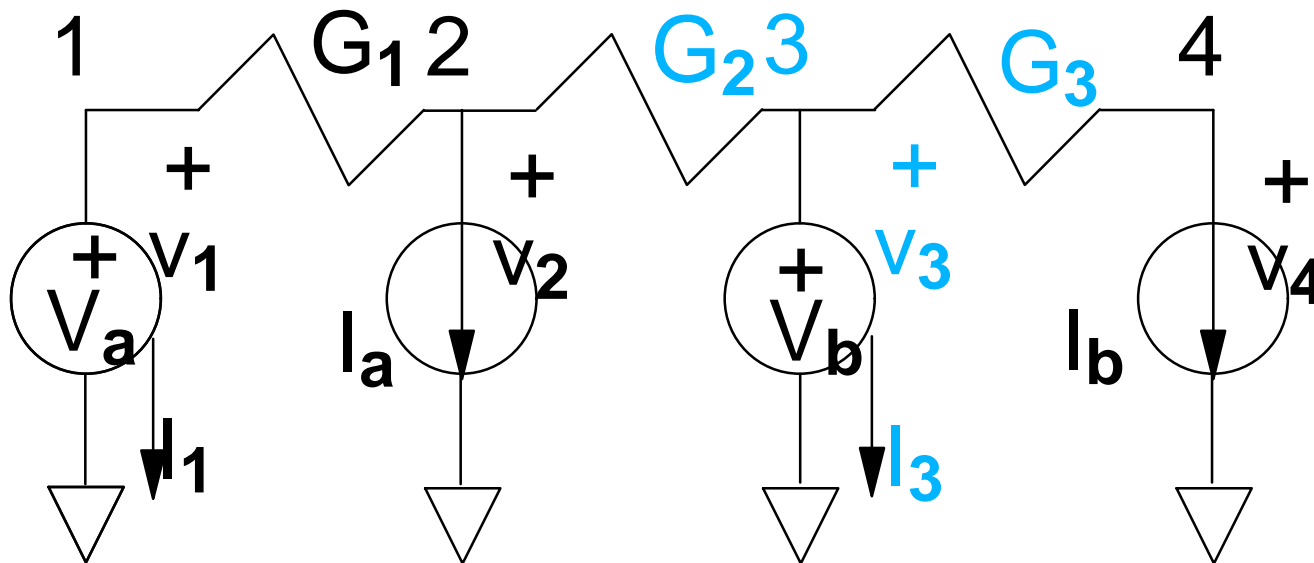
$$(V_3 - V_2)G_2 + (V_3 - V_4)G_3 + I_3 = 0$$



Circuit Analysis: Example

- Applying KCL at node 4

$$(V_4 - V_3)G_3 + I_b = 0$$

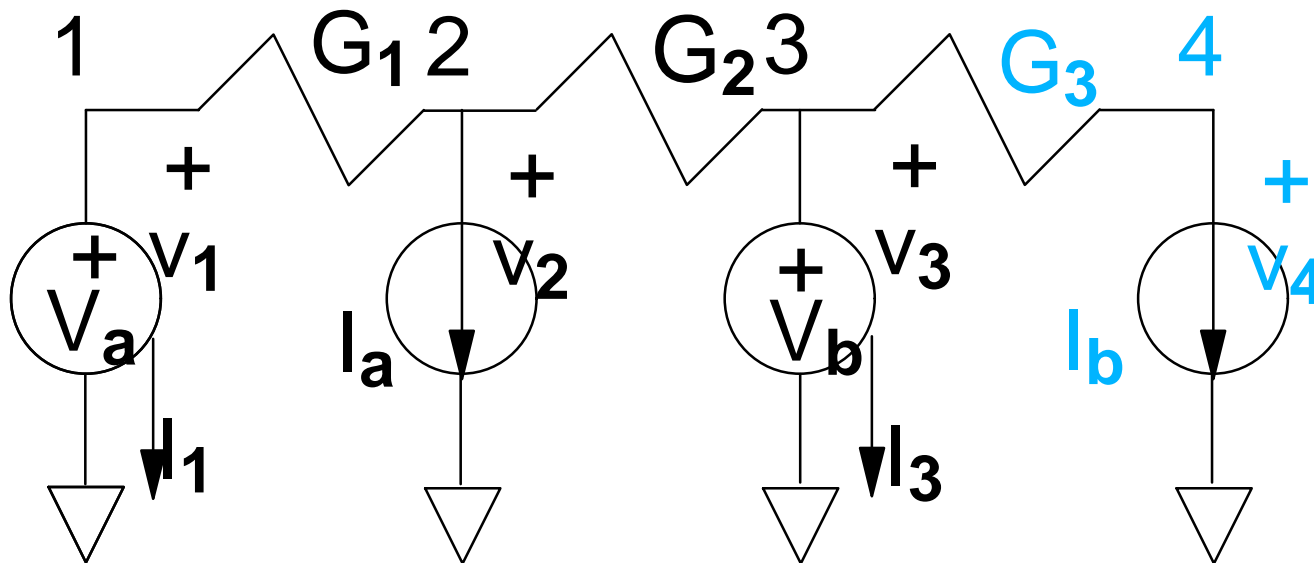

Circuit Example

- Collecting these equations, we get

$$\begin{bmatrix}
 G1 & -G1 & 0 & 0 & 1 & 0 \\
 -G2 & G1+G2 & -G2 & 0 & 0 & 0 \\
 0 & -G2 & G2+G3 & -G3 & 0 & 1 \\
 0 & 0 & -G3 & G3 & 0 & 0 \\
 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 I_1 \\
 I_2
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 I_a \\
 0 \\
 I_b \\
 V_1 \\
 V_2
 \end{bmatrix}$$

Voltage at load Pad voltages

Circuit Analysis: Example

- In general, these circuits have the form:

$$\mathbf{GV} = \mathbf{I}$$

- ▶ \mathbf{G} is called the "Admittance" matrix
- ▶ pad voltage sources appear as elements in \mathbf{I}
- ▶ Node voltages are solved as elements of \mathbf{V}
- Solvable in linear time & memory
- Effect of adding or subtracting voltage sources calculated in constant time

Quality of Assignment

- Node Voltages are within a particular range

$$V_{\min} < V_i < V_{\max}$$

- Currents on power grid must not exceed their capacity to carry it

$$I_{\max} > G_{ik}(V_i - V_k)$$

Formulation

Given Pads $\{C_1 \dots C_n\}$ and power levels $\{0, P_1 \dots P_k\}$ derive an unique assignment of P_i for every C_u , such that the demand requirements on P_i

$$V_{\min P_i} < D_{P_i} V < V_{\max P_i}$$

are met, where D_{P_i} is the "demand" matrix with V satisfying the relationship


$$G_{P_i} V = I_{P_i}$$

Dimension of the Problem

- Number of Pads : 1000s
- Number of Voltage Levels : 2-4
- Number of Load Nodes: ~10-30 Million
- Dimension of Demand matrix: constant factor (~4-5) in number of load nodes

Power Grid Design

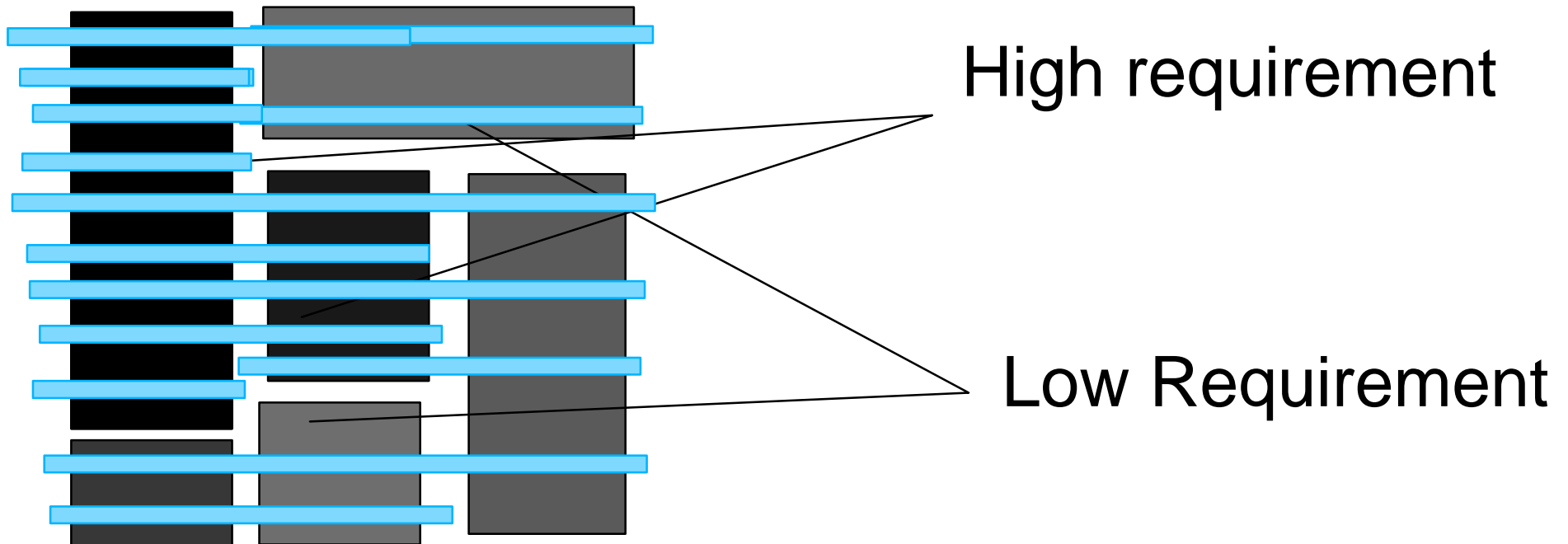- Different parts have different load requirements
- Desirable to minimise metal usage in low demand regions



Power Grid Requirements

- Different Metal Usage strategies for a given load region possible
- Leads to multiple possibilities for the "Admittance" matrix **G**

Power Grid Requirements

In addition to Pad assignment, optimise the grid's metal usage by selecting a **G** matrix from $\{G_{1P_i} \dots G_{mP_i}\}$ for each Power level P_i

Other Issues: Time Dependency

- Current model is static, in reality need voltages over multiple time points
 - ▶ Causes the relationship to become $GV + CV' = I$ (V' is the derivative)
- Solved by converting to difference equations and using trapezoidal methods
- Require current through Pads (I_1 & I_3 in example) to not exceed Pad's capacity